

Operating Systems


Ahmad Yoosofan

University of Kashan

<https://yoosofan.github.io/en/>

Yoosofan Imaginary Computer (YIC)

Based on Morris Mano's famous book

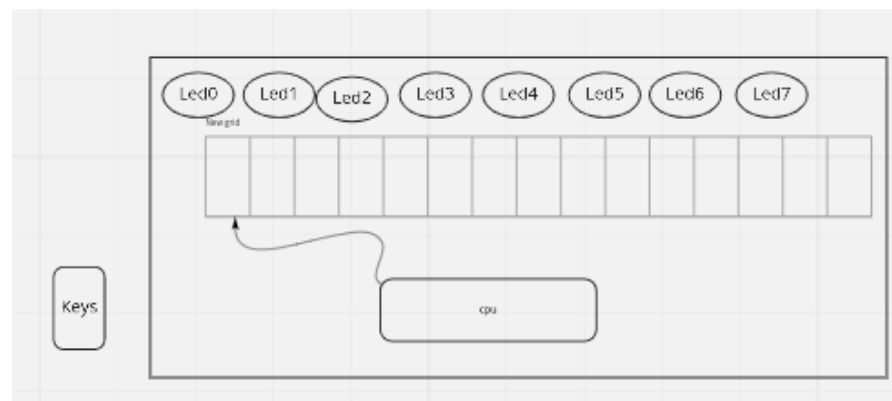

YIC 10, Instruction Set(I)

AND: Logical AND memory with AC
ADD: Arithmetic ADD memory with AC
LDA: Load from memory to AC
STA: Store AC to memory
BUN: Branch unconditional
ISZ: Increment and skip if zero
CLA: Clear AC
CLE: Clear E
CMA: Complement AC
CME: Complement E
CIR: Circulate right (AC and E)
CIL: Circulate left (AC and E)

INC: Increment AC
SPA: Skip if positive AC
SNA: Skip if negative AC
SZA: Skip if zero AC
SZE: Skip if zero E
HLT: Halt
OUT: Output a character from AC
SKO: Skip if output flag
NOP: No operation

YIC 10, Instruction Set Binary(II)

AND:	00001
ADD:	00010
LDA:	00011
STA:	00100
BUN:	00101
ISZ:	00110
CLA:	00111
CLE:	01000
CMA:	01001
CME:	01010
CIR:	01011
CIL:	01100

INC:	01101
SPA:	01110
SNA:	01111
SZA:	10000
SZE:	10001
HLT:	10010
OUT:	10011
SKO:	10100
NOP:	10101

hex pad connect to microcontroller

<https://www.circuitstoday.com/interfacing-hex-keypad-to-8051>









<https://circuitdigest.com/microcontroller-projects/keypad-interfacing-with-avr-atmega32>


Example

- <https://github.com/yoosofan/mano-computer-simulator-js>
- <https://yoosofan.github.io/mano-computer-simulator-js/>
- <https://github.com/Naheel-Azawy/Simple-Computer-Simulator/blob/master/test/test-symbolic>
- <https://github.com/Naheel-Azawy/Simple-Computer-Simulator/blob/master/test/test>
- <https://github.com/Naheel-Azawy/Simple-Computer-Simulator/tree/master/test>


Other assembly

- <http://imrannazar.com/arm-opcode-map>
- <https://iitd-plos.github.io/col718/ref/arm-instructionset.pdf>
- https://wiki.osdev.org/X86-64_Instruction_Encoding
- https://cs.brown.edu/courses/cs033/docs/guides/x64_cheatsheet.pdf
- <https://sites.google.com/site/nttrungmtwiki/home/rce/assembly-language/x64-opcode-and-instruction-reference-home>
- <http://ref.x86asm.net/coder64.html>
- arm 32 opcodes
- <http://z80-heaven.wikidot.com/instructions-set:ld>
- <http://z80-heaven.wikidot.com/opcode-reference-chart>
- <https://smallcomputercentral.files.wordpress.com/2017/12/asm80-com-tutorial-e1-0-01.pdf>
- <https://stackoverflow.com/questions/22838444/convert-an-8bit-number-to-hex-in-z80-assembler>
- <https://www.vcfed.org/forum/forum/technical-support/vintage-computer-programming/76419-z80-hello-world-example-in-hex>
- <https://www.cemetech.net/forum/viewtopic.php?t=15710&start=0>
- z80 assembly codes

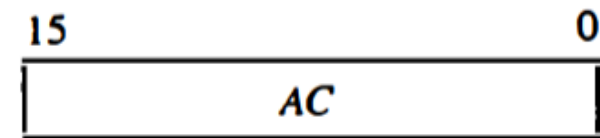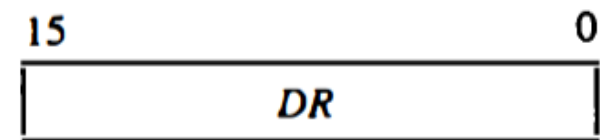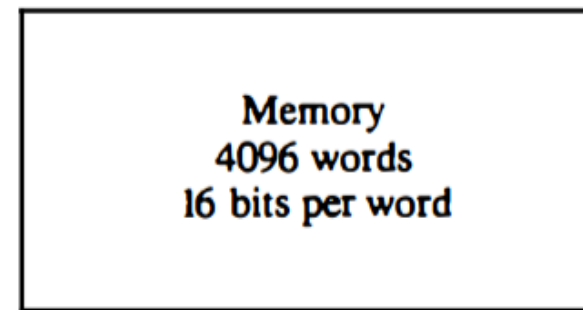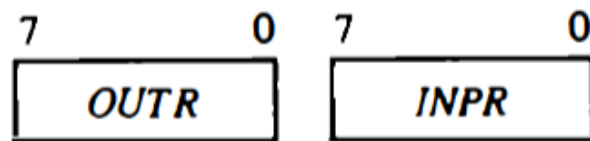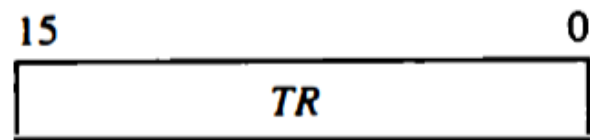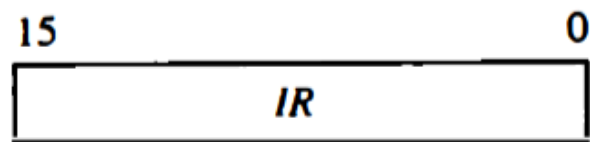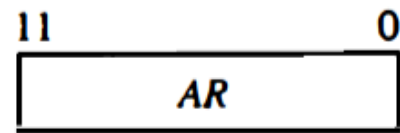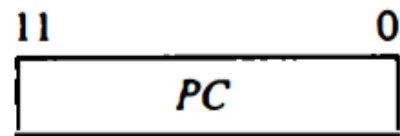


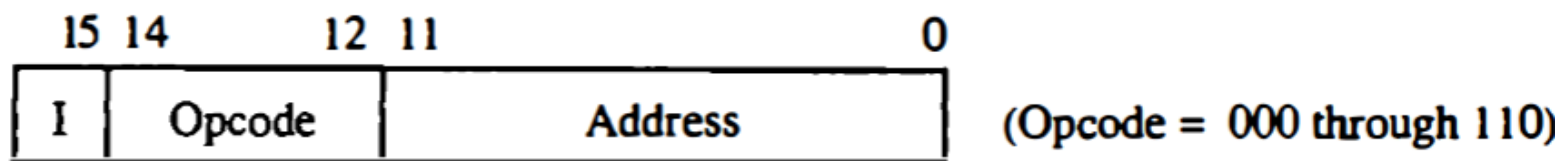

(a) Memory – reference instruction

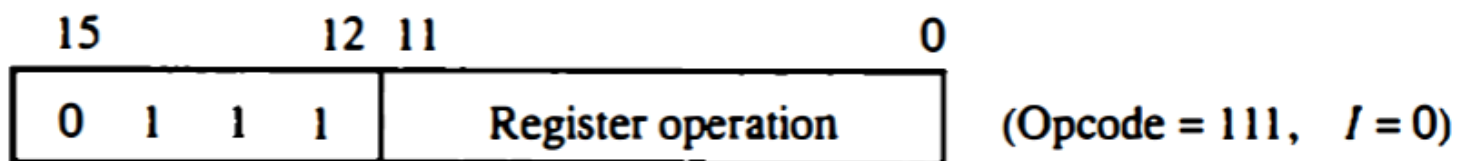

(b) Register – reference instruction

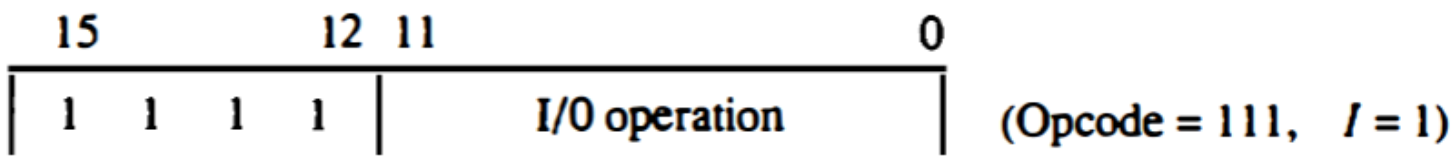

(c) Input – output instruction

00101	00000	1010
00110	00000	1100
00111	00000	1110
01000		
00000		

اگر حداکثر ۳۲ دستور داشته باشیم پس پنج بیت برای دستورها نیاز داریم برای سادگی فرض می‌کنیم که طول همه دستورها یکسان است یعنی هم دو بایت را می‌گیرند فرض کنید دستورها پنج بیت نیاز دارند پس ۱۱ بیت برای آدرس

حداکثر حافظه این کامپیوتر چقدر می‌تواند باشد. اگر بخواهیم بایتی آدرس دهی کنیم

$$2^{11} = 2\text{kB}$$

B = Byte

اگر آدرس‌دهی را دو بایتی در نظر بگیریم

$$4\text{kB (word = 2 byte)}$$

Output

LED

seven segment


- <https://www.rapidtables.com/convert/number/hex-to-binary.html>
- convert hex to binary
- <https://clrhme.org/asm/>

Output Problem


```
lda a
add b
sta c
out
hlt
a, 5
b, 2
c, 0
```

```
.....
.....
LB1: out
     sko
     bun LB1
.....
.....
```


Simple LED

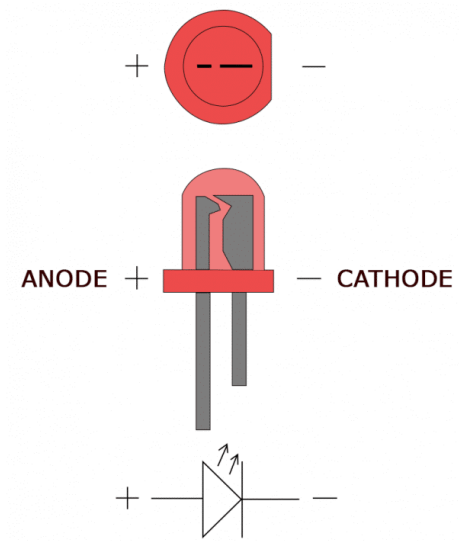

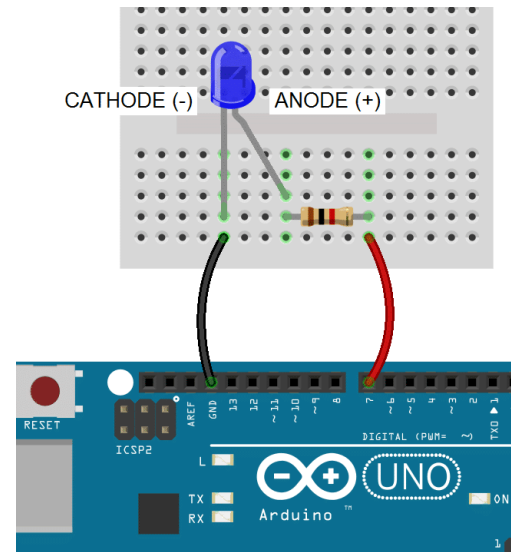
[circuitbasics](http://circuitbasics.com)



Seven segment display

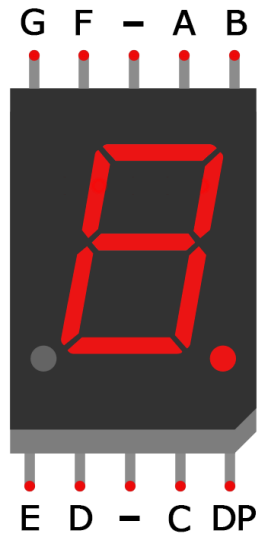

[circuitbasics](#) [askingthelot](#)

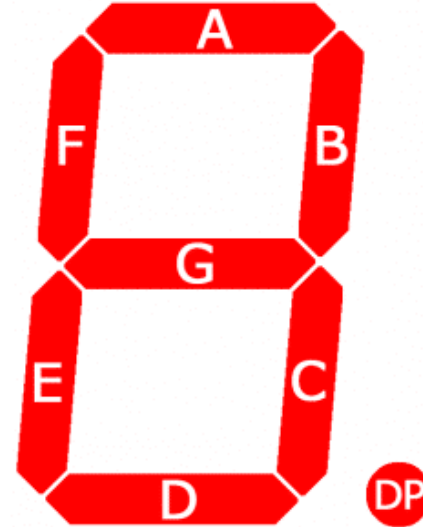


[youtu.be](#) [element14](#)

Imaginary Computer

- Consider it as real a computer
- Think about business plan
- Consider customers' need
- Consider other companies

YIC 30, Seven segment

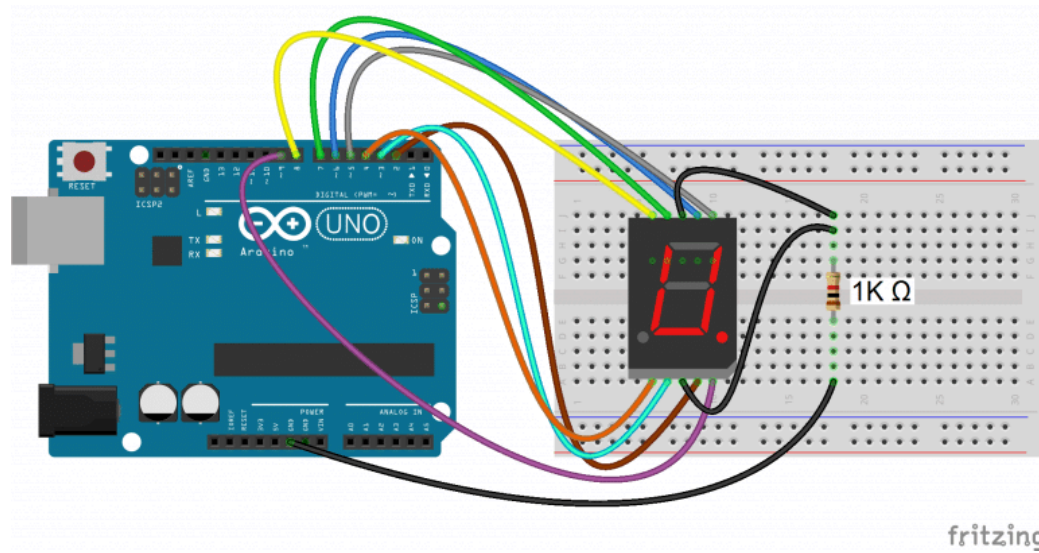


[circuitbasics](https://www.circuitbasics.com/)



Issues of YIC 30

- Convert binary number to 7 segment code
- Old codes only LED
- LED & seven segment
- Changing CPU
- Cost of changes
- Just one 7 segment ?
- for every output, seven segment code should be added

Hardware instead of Software

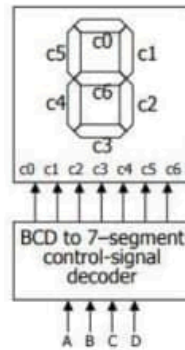
[illegible]

4 Digit 7-Segment Displays

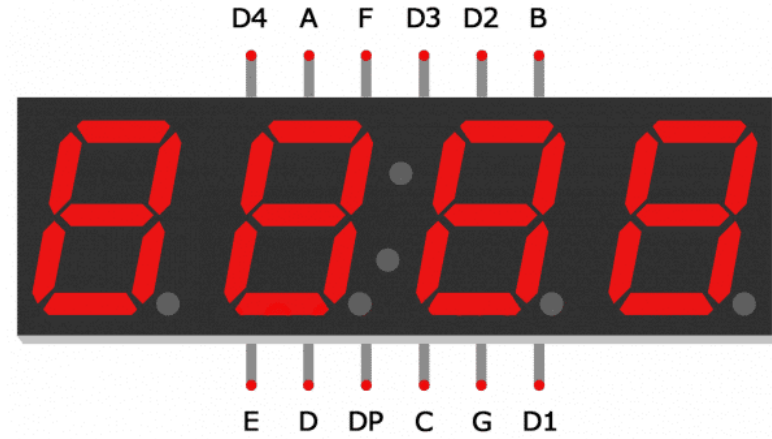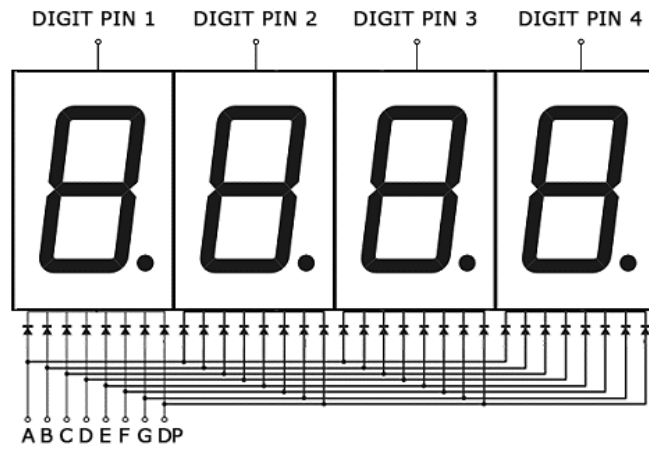

[circuitbasics](http://circuitbasics.com)

Connecting 4 Digit 7-Segment Displays

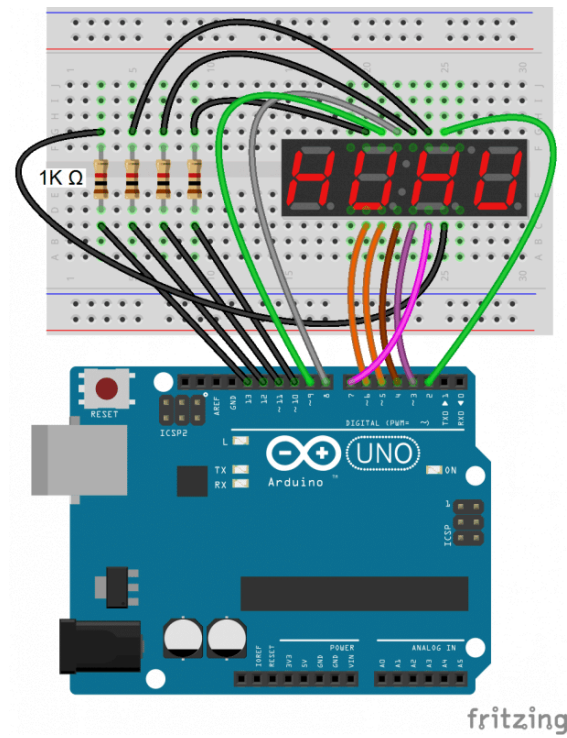

Arduino Print 4 to 7-segment

```
#include "SevSeg.h"
SevSeg sevseg;

void setup(){
  byte numDigits = 1;
  byte digitPins[] = {};
  byte segmentPins[] =
    {6, 5, 2, 3, 4, 7, 8, 9};
  bool resistorsOnSegments = true;

  byte hardwareConfig = COMMON_CATHODE;
  sevseg.begin(hardwareConfig,
    numDigits, digitPins, segmentPins,
    resistorsOnSegments
  );
  sevseg.setBrightness(90);
}


void loop(){
  sevseg.setNumber(4);
  sevseg.refreshDisplay();
}
```

Segment Pin	Arduino Pin
A	6
B	5
C	2
D	3
E	4
F	7
G	8
DP	9


[circuitbasics](https://circuitbasics.com/arduino-sevseg-library/)

YIC 40 - BSA

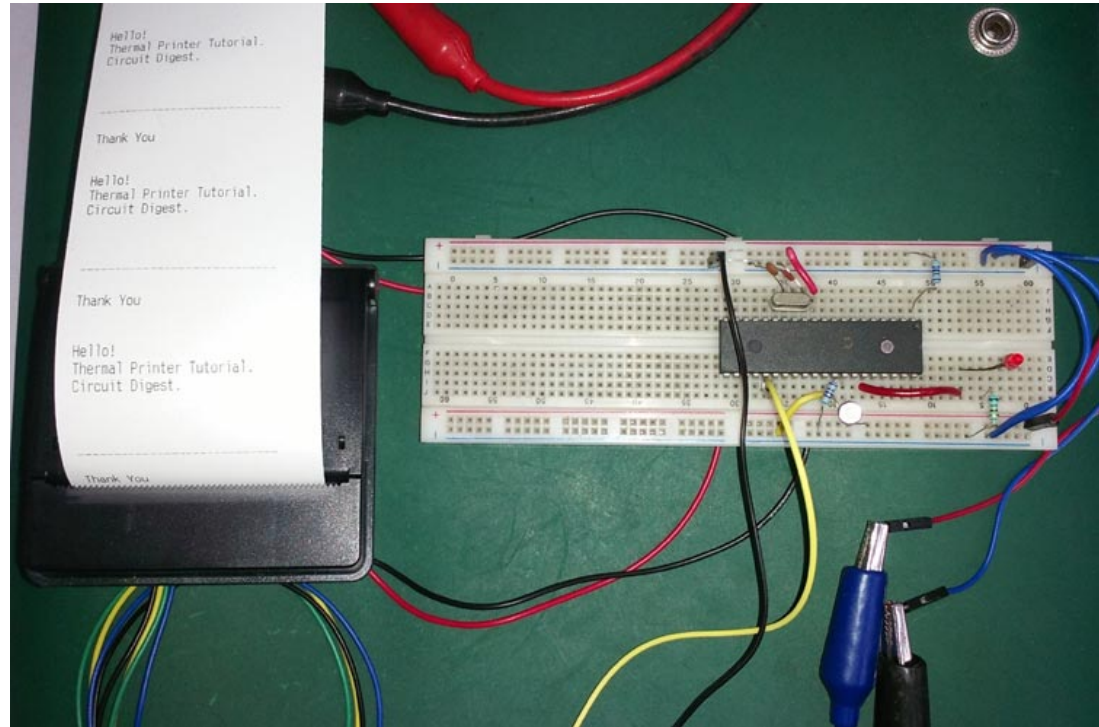
1. LED output code
2. 7 segment code
3. Printer
4. output selector
5. Adding porecedures
6. Device Drivers
7. Adding more devices
8. No error checking
9. Send data
10. API (protocol)



Printer Routine

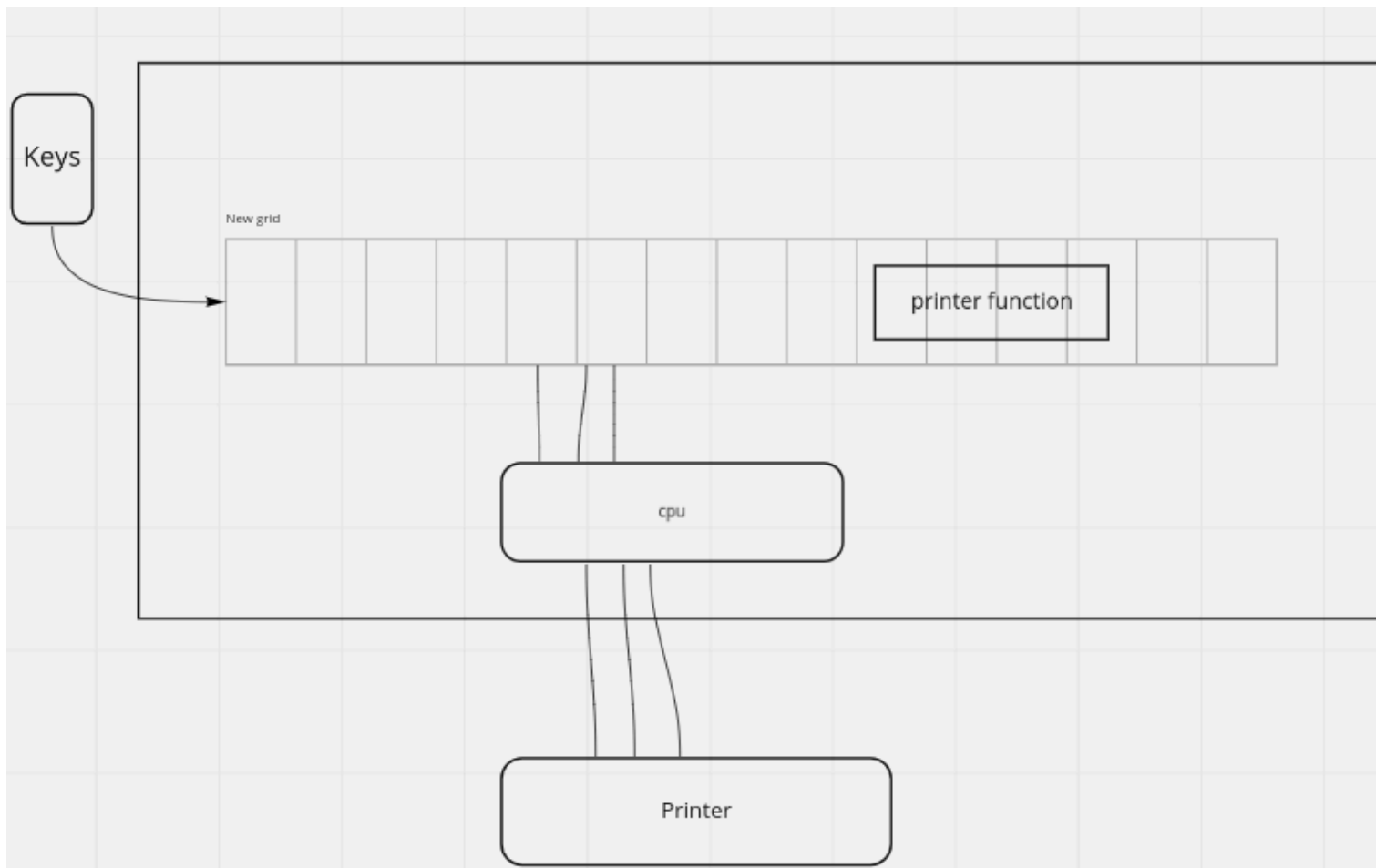

Adding procedurs to memory

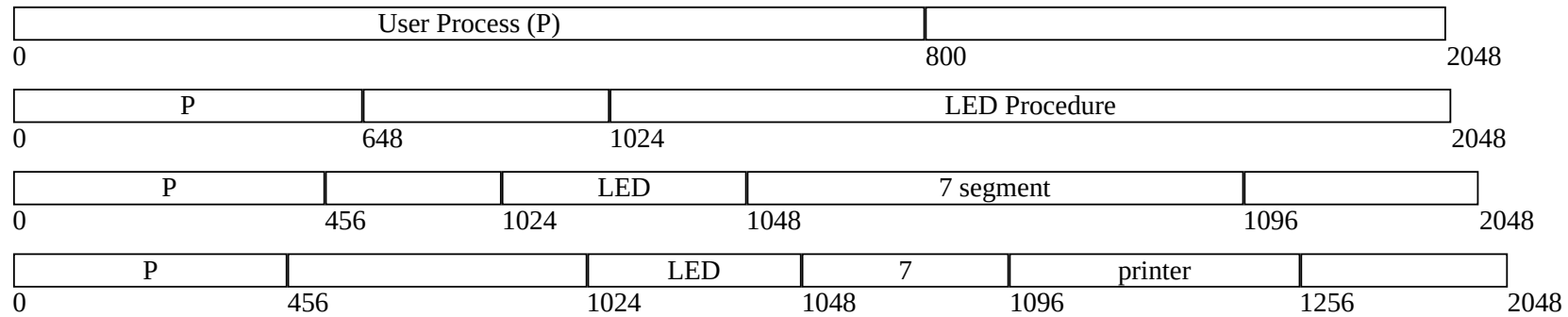

Users (programmers) should know where these precedures are

YIC50 - Array of Addresses

P		array	LED	7	printer		
0	456	1000	1024	1048	1096	1256	2048

Array

1024	1048	1096	1256	
0	1	2	3	4

indirect BSA

User chooses between old cpu or new one

YIC60 - Input Device (Card Reader)

1. Card Reader
2. Necessary Loops
3. Check Errors
4. Polling Method

- Hollerith and IBM keypunches, 1890
- IBM 011 Electric Key Punch(1923)
- IBM Type 032 Printing Punch(1935)
- A Key Punch Room in the 1960s



card punch



card reader



1		ORG	0
2	START,	BSA	READ1
3		STA	BYTE1
4		LDA	BYTE1
5		BSZ	OUTCH
6		HLT	
7			
8	READ1,	HEX	0
9	RDCNT,	SKI	
10		BUN	RDCNT
11		INP	
12		BUN	(READ1)
13			
14	OUTCH,	HEX	0
15	OUTPR,	SKO	
16		BUN	OUTPR
17		OUT	
18		BUN	(OUTCH)
19			
20	BYTE1,	DEC	0
21		END	

Simple Input Output Code - YIC60

1		ORG	0
2	START,	BSA	INPUT
3		STA	NUM1
4			
5		BSA	INPUT
6		STA	NUM2
7			
8		LDA	NUM1
9		ADD	NUM2
10		STA	RESULT
11			
12		BSA	OUTPUT
13			
14		HLT	

15	INPUT,	HEX	0
16	POLL,	SKI	
17		BUN	POLL
18		INP	
19		BUN	(INPUT)
20			
21	OUTPUT,	HEX	0
22	OUT_P,	SKO	
23		BUN	OUT_P
24		OUT	
25		BUN	(OUTPUT)
26			
27	// Data Section		
28	NUM1,	DEC	0
29	NUM2,	DEC	0
30	RESULT,	DEC	0
31			
32		END	

YIC60 - Array of Addresses

P		array	LED	7	printer		
0	456	1000	1024	1048	1096	1256	2048

Array

	1024		1048		1096		1256	
0		1		2		3		4

YIC60 code with array(I)

```
1  START   BSA    (PVT_INPUT)
2          STA    NUM1
3          BSA    (PVT_INPUT)
4          STA    NUM2
5          LDA    NUM1
6          ADD    NUM2
7          STA    RESULT
8          BSA    (PVT_OUTPUT)
9          HLT
10 NUM1,    DEC    0
11 NUM2,    DEC    0
12 RESULT,  DEC    0
13
14          ORG    150
15 PVT_INPUT,  HEX 200
16 PVT_OUTPUT,  HEX 220
17
18          ORG    200
19 INPUT,    HEX 0
20 IN_POLL,  SKI
21          BUN    IN_POLL
22          INP
23          BUN    (INPUT)
```

```
19          ORG    220
20 OUTPUT,   HEX 0
21          STA    TEMP_OUT
22
23 OUT_POLL, SK0
24          BUN    OUT_POLL
25          LDA    TEMP_OUT
26          OUT
27          BSA    (PVT_DELAY)
28          BUN    (OUTPUT)
29
30          ORG    240
31 DELAY,     HEX 0
32          LDA    DELAY_COUNT
33          STA    DELAY_CTR
34
35 DELAY_LOOP,
36          LDA    DELAY_CTR
```

YIC60 code with array(II)

```
1  DELAY,  HEX      0
2          LDA      DELAY_COUNT
3          STA      DELAY_CTR
4
5  DELAY_LOOP,
6          LDA      DELAY_CTR
7          SZA
8          BUN      CONTINUE_DELAY
9          BUN      (DELAY)
10
11 CONTINUE_DELAY,
12         DEC
13         STA      DELAY_CTR
14         BUN      DELAY_LOOP
15
16         ORG      300
17 TEMP_OUT,  DEC      0
18 DELAY_COUNT, DEC    10
```

```
21 DELAY_CTR,  DEC      0
22 PVT_DELAY,  HEX     52
23          END
```


YIC70 - Adding Loader

Loader	user process		array	LED	7	printer	Card Reader		
0	100	556	1000	1024	1048	1096	1256	1450	2048


Array

1024	1048	1096	1256	
0	1	2	3	4

1		ORG	0
2	START,	BSA	READ_COUNT
3		STA	BYTE_COUNT
4		BSA	INIT_LOAD
5		BSA	LOAD_LOOP
6		BSA	EXECUTE
7		BUN	0
8		HLT	
9			
10	READ_COUNT,	HEX	0
11	RD_CNT,	SKI	
12		BUN	RD_CNT
13		INP	
14		BUN	READ_COUNT I
15			
16	INIT_LOAD,	HEX	0
17		LDA	ZERO
18		STA	CURRENT_IDX
19		BUN	INIT_LOAD I
20			
21	LOAD_LOOP,	HEX	0
22		LDA	CURRENT_IDX
23		SUB	BYTE_COUNT
24		SPA	
25		BUN	LOAD_BYTE
26		BUN	LOAD_LOOP I
27			
28	LOAD_BYTE,		
29		BSA	READ_BYTE
30		STA	TEMP_BYTE


32		LDA	LOAD_PTR
33		ADD	CURRENT_IDX
34		STA	STORE_PTR
35		LDA	TEMP_BYTE
36		STA	STORE_PTR I
37		LDA	CURRENT_IDX
38		INC	
39		STA	CURRENT_IDX
40		BUN	LOAD_LOOP
41			
42	READ_BYTE,	HEX	0
43	RD_BYT,	SKI	
44		BUN	RD_BYT
45		INP	
46		BUN	READ_BYTE I
47			
48		ORG	128
49	EXECUTE,	HEX	0
50			
51		LDA	ZERO
52		STA	RESULT
53		BUN	EXECUTE I
54			
55		ORG	64
56	ZERO,	DEC	0
57	BYTE_COUNT,	DEC	0
58	LOAD_PTR,	HEX	128
59	CURRENT_IDX,	DEC	0
60	TEMP_BYTE,	DEC	0
61	STORE_PTR,	HEX	0
62	RESULT,	DEC	0

YIC75 Relative Address

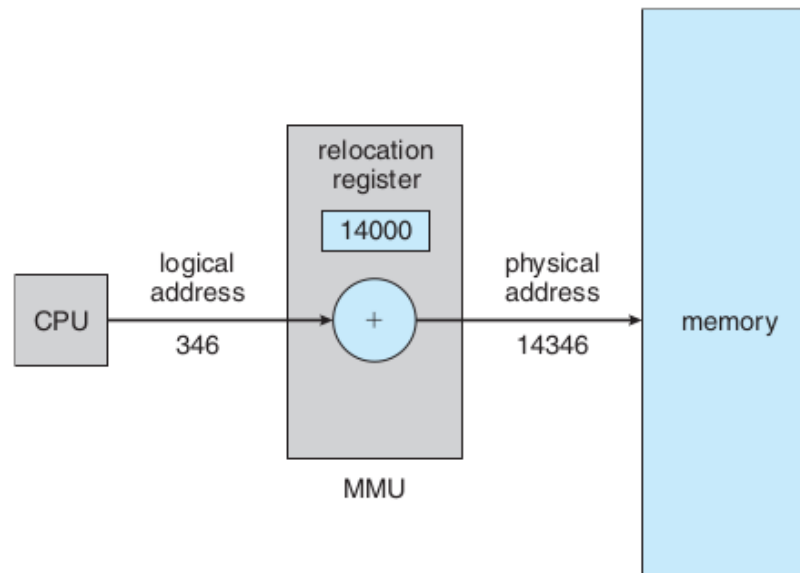


address binding, absolute and relocate loader

Symbolic
addresses

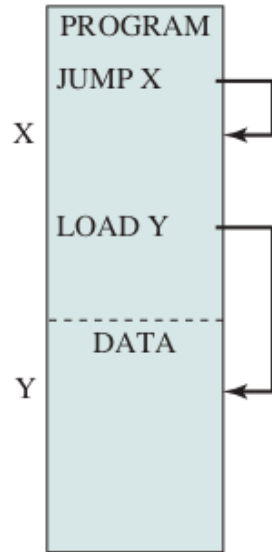


(a) Object module

Absolute
addresses

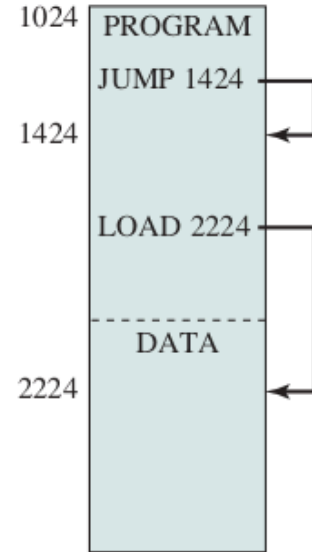


(b) Absolute load module

Relative
addresses

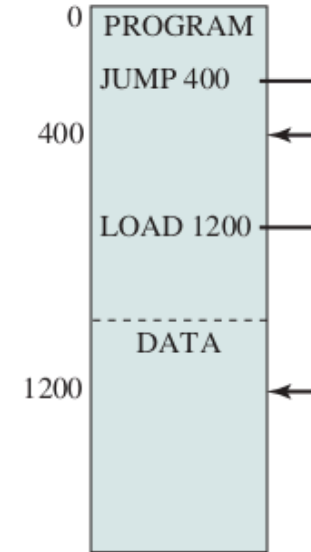


(c) Relative load module

Main memory
addresses

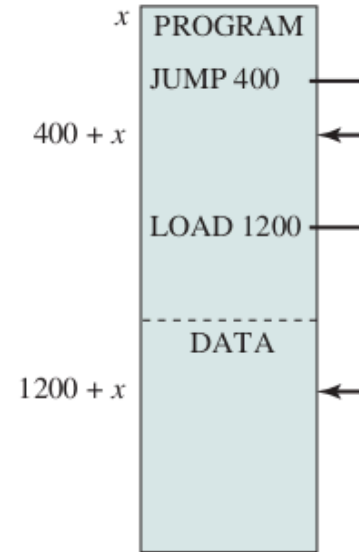

(d) Relative load module
loaded into main memory
starting at location x

YIC80 - Interrupt

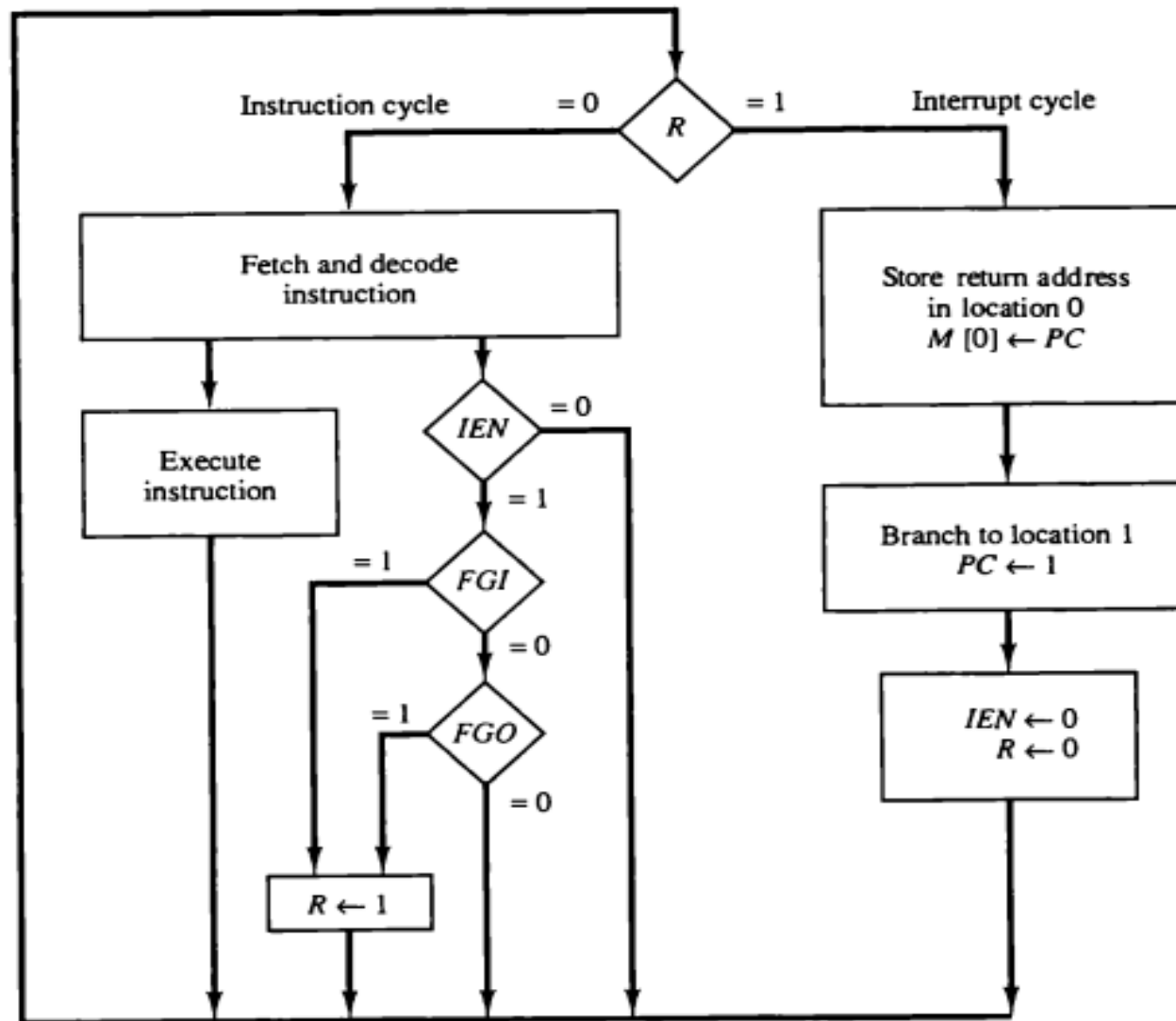

Interrupt-Driven Program

1		ORG	0
2		BUN	MAIN
3		BUN	ISR
4			
5	MAIN,	LDA	ZERO
6		STA	COUNT
7		ION	
8			
9	WORK,	LDA	COUNT
10		INC	
11		STA	COUNT
12		BUN	WORK
13			
14	ISR,	STA	SAVE
15		BSA	IO
16		LDA	SAVE
17		ION	
18		BUN	0 I

20	IO,	HEX	0
21		SKI	
22		BUN	OUTPUT
23		INP	
24		STA	BUFFER
25		BUN	IO I
26	OUTPUT,	SKO	
27		BUN	IO I
28		OUT	
29		BUN	IO I
30			
31	ZERO,	DEC	0
32	COUNT,	DEC	0
33	SAVE,	DEC	0
34	BUFFER,	DEC	0
35		END	

Save E flag

Input, Add and Output

1		ORG	0
2		BUN	MAIN
3		BUN	ISR
4	MAIN,	LDA	ZERO
5		STA	READY
6		ION	
7	WAIT,	LDA	READY
8		SZA	
9		BUN	PROCESS
10		BUN	WAIT
11	PROCESS,	LDA	BUFFER
12		ADD	TEN
13		STA	BUFFER
14		BSA	OUT_SUB
15		HLT	
16			
17	OUT_SUB,	HEX	0
18	POLL_0,	SKO	
19		BUN	POLL_0
20		LDA	BUFFER
21		OUT	
22		BUN	OUT_SUB I
23			
24	ISR,	BSA	SAVE_SUB
25		SKI	
26		BUN	ISR_EXIT

28		INP	
29		STA	BUFFER
30		LDA	ONE
31		STA	READY
32			
33	ISR_EXIT,	BSA	RSTR_SUB
34		ION	
35		BUN	0 I
36			
37	SAVE_SUB,	HEX	0
38		STA	TEMP_AC
39		CIL	
40		STA	TEMP_E
41		BUN	SAVE_SUB I
42			
43	RSTR_SUB,	HEX	0
44		LDA	TEMP_E
45		CIR	
46		LDA	TEMP_AC
47		BUN	RSTR_SUB I
48			
49	ZERO,	DEC	0
50	ONE,	DEC	1
51	TEN,	DEC	10
52	READY,	DEC	0
53	BUFFER,	DEC	0
54	TEMP_AC,	DEC	0
55	TEMP_E,	DEC	0

	Loader	READ	WRITE	ISR	DATA	user process	
0	2	100	150	200	250	300	1024

```

1      BUN    LOADER_MAIN
2      BUN    ISR
3  LOADER_MAIN, ION
4  LOAD_LOOP, BSA  READ_WORD
5      STA    PROG_SIZE
6      BSA    LOAD_PROGRAM
7      BSA    PROGRAM_BASE
8      BUN    LOAD_LOOP
9  LOAD_PROGRAM, HEX 0
10     LDA    ZERO
11     STA    LOAD_INDEX
12  LOAD_PROGRAM_LOOP,
13     LDA    LOAD_INDEX
14     SUB    PROG_SIZE
15     SPA
16     BUN    LOAD_DONE
17     BSA    READ_WORD
18     STA    TEMP_DATA
19     LDA    LOAD_INDEX
20     ADD    PROGRAM_BASE
21     STA    TEMP_ADDR
22     LDA    TEMP_DATA
23     STA    TEMP_ADDR I
24     LDA    LOAD_INDEX
25     INC
26     STA    LOAD_INDEX
27     BUN    LOAD_PROGRAM_LOOP
28  LOAD_DONE, BUN LOAD_PROGRAM I
29     ORG    100
30  READ_WORD, HEX 0
31  WAIT_FOR_INPUT, LDA INPUT_READY
32     SZA

```

```

33     BUN    HAVE_INPUT
34     BUN    WAIT_FOR_INPUT
35  HAVE_INPUT,
36     LDA    INPUT_BUFFER
37     STA    TEMP_DATA
38     LDA    ZERO
39     STA    INPUT_READY
40     LDA    TEMP_DATA
41     BUN    READ_WORD I
42     ORG    150
43  WRITE_WORD, HEX 0
44     STA    OUTPUT_DATA
45     LDA    ONE
46     STA    OUTPUT_PENDING
47  WAIT_FOR_OUTPUT,
48     LDA    OUTPUT_PENDING
49     SZA
50     BUN    WAIT_FOR_OUTPUT
51     BUN    WRITE_WORD I
52     ORG    200
53  ISR, STA    SAVE_AC
54     SKI
55     BUN    CHECK_OUTPUT
56     INP
57     STA    INPUT_BUFFER
58     LDA    ONE
59     STA    INPUT_READY
60     BUN    ISR_EXIT
61  CHECK_OUTPUT, SKO
62     BUN    ISR_EXIT
63     LDA    OUTPUT_PENDING
64     SZA

```

```

65     BUN    PERFORM_OUTPUT
66     BUN    ISR_EXIT
67  PERFORM_OUTPUT,
68     LDA    OUTPUT_DATA
69     OUT
70     LDA    ZERO
71     STA    OUTPUT_PENDING
72  ISR_EXIT, LDA  SAVE_AC
73     BUN    0 I
74     ORG    250
75  ZERO, DEC 0
76  ONE, DEC 1
77  PROG_SIZE, DEC 0
78  LOAD_INDEX, DEC 0
79  TEMP_ADDR, HEX 0
80  TEMP_DATA, DEC 0
81  INPUT_BUFFER, DEC 0
82  INPUT_READY, DEC 0
83  OUTPUT_DATA, DEC 0
84  OUTPUT_PENDING, DEC 0
85  SAVE_AC, DEC 0
86  PROGRAM_BASE, HEX 300
87     END
88
89     ORG 300 ; User program
90  USER_ENTRY, HEX 0
91     BSA 100
92     ADD TEN
93     BSA 150
94     BUN USER_ENTRY I
95     TEN, DEC 10
96     END

```


Other Loader Samples

Advanced: Buffered Input with BSA Subroutines

src/in/Interrupt_Driven_Program_with_BSA_Subroutines_Advanced_with_buffer.asm

src/in/Interrupt_Driven_Program_with_BSA_Subroutines_Advanced_with_buffer_comments.asm

Enhanced bootstrap loader with error checking

src/in/Bootstrap_Loader_Program_More_Robust_Version_with_Error_Checking.asm

Relocating Bootstrap Loader with Base Register

src/in/loader4_base_register_comments.asm

Simple Bootstrap Loader with Absolute Addressing

src/in/loader7_interrupt_Simple_Bootstrap_Loader_with_Absolute_Addresssing.asm

src/in/loader7_interrupt_Simple_Bootstrap_Loader_with_Absolute_Addresssing_comments.asm

src/in/loader7_user_program_comments.asm

src/in/loader7_user_program.asm

Uses interrupt-driven I/O instead of polling

src/in/loader10_interrupt.asm

src/in/loader10_interrupt_comments.asm

Interrupt-driven program that gets loaded

src/in/loader10_loaded_program.asm

src/in/loader10_loaded_program_comments.asm

Review YICs

Before Loader

1. Connect memory to power
2. Connect HEX Pad keyboard to memory.
3. Enter machine code of OS Routines to memory
4. Connect output device(printer) to CPU
5. Connect input device(card reader) to CPU
6. Enter machine code of next customer to memory
7. Disconnect HEX Pad keyboard and memory.
8. Connect CPU to memory
9. Turn on CPU
10. Runnig customer code
11. HLT at the end of customer code (Turn off CPU)
12. Give output(s) to Customer
13. Disconnect CPU and memory
14. Connect HEX Pad keyboard to memory.
15. Back to step 6


After Loader

1. Connect memory to power
2. Connect HEX Pad keyboard to memory.
3. Enter machine code of OS Routines to memory
4. Connect output device(printer) to CPU
5. Connect input device(card reader) to CPU
6. Disconnect HEX Pad keyboard and memory.
7. Connect CPU to memory
8. Turn on CPU
9. Runnig loader of OS
10. Read size of customer code from input
11. Read a custmer code from input
12. Write the customer code to memory
13. Go 11 to until the size of customer code
14. Jump or BSA to customer code
15. Runnig customer code
16. BUN to loader at the end of customer code
17. Give output(s) to Customer

Relative Address Problem

- Normal execution
 - Logical Address
 - Base or Relocation Register
 - Physical address $\leftarrow$ PC + Base
 - AR $\leftarrow$ Base + PC
 - Kernel Mode
 - UMD: Change CPU mode to user
 - mode = 1, a flag in CPU Like C
- Kernel
 - Interrupt Service Routine (ISR)
 - Boot
 - Loader
 - OS routines and libraries
 - Effective address = logical address
 - KMD: change CPU mode to kernel
 - mode = 0
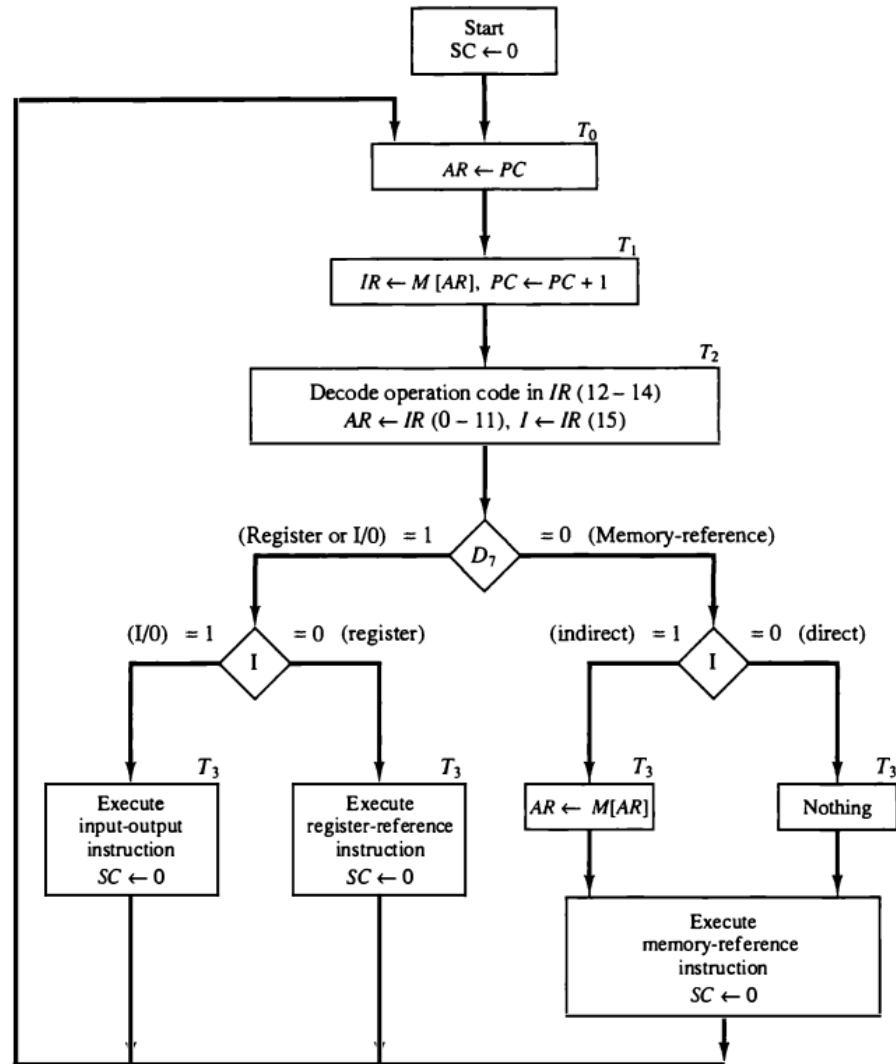
```
1  ORG 0
2  BUN  LOADER
3  BUN  ISR
4  LOADER, ION
5  LOOP, BSA READ_WORD
6  STA  SIZE
7  BSA  LOAD
8  UMD
9  BSA  300
10 BUN  LOOP
11
12 ; ISR
13 ; Routines
14 END
15
16 ORG 300 ; User program
17 UPRG, HEX 0
18 BSA  100
19 ADD  TEN
20 BSA  150
21 BUN  300 I
22 TEN, DEC 10
23 END
```



YIC90 Requirements

1. Adding Base Register
2. Adding CPU mode flag
3. interrupt micro-operations
 1. $M[0] \leftarrow PC$
 2. $PC \leftarrow 1$
 3. $IEN \leftarrow 0$
 4. $MODE \leftarrow 0$
4. Physical Address = $AR + (MODE * Base)$
5. ATB (AC to Base)
6. Return from Interrupt (RTI)
 1. t3: $AR \leftarrow 0$
 2. t4: $DR \leftarrow M[AR]$
 3. t5:
 1. $PC \leftarrow DR$
 2. $MODE \leftarrow 1$
 3. $IEN \leftarrow 1$
 4. $SC \leftarrow 0$
7. Return to Kernel
 1. $M[30] \leftarrow PC$
 2. $PC \leftarrow 31$
 3. $MODE \leftarrow 0$
 4. $IEN \leftarrow 0$
8. System Call using RTK
 1. AC = 0: exit program
 2. AC = 1: Read
 3. AC = 2: Write
9. Mailbox: Shared Memory.

```
1  BUN BOOT
2  BUN ISR
3
4  ORG 030
5  HEX 0
6  BUN SYSCALL
7  BOOT, CLA
8  ; Load loop
9  ; jump to user
10 L_RUN, LDA PROG_BASE
11      ATB
12      CLA
13      STA 0
14      RTI
15 SYSCALL, SZA
16      BUN SC_CHECK
17      BUN BOOT
```

```
1  ORG 300
2  LDA C_RD
3  RTK
4  LDA MAILBOX
5  ADD FIVE
6  STA MAILBOX
7  LDA C_WR
8  RTK
9  CLA
10 RTK ;src/yic/yic90...
11 C_RD, DEC 1
12 C_WR, DEC 2
13 FIVE, DEC 5
14      ORG 700
15 MAILBOX, DEC 0
```

	BOOT	LOADER	RUN	SYSCALL	ISR	DATA	user process	MAIL	
0	32	60	94	104	172	220	300	1000	1024

```

1      ORG 0
2      BUN BOOT
3      BUN ISR
4
5      ORG 030
6      HEX 0
7      BUN SYSCALL
8
9  BOOT,  CLA
10      STA IN_READY
11      STA OUT_READY
12      ION
13
14  GETSZ, LDA IN_READY
15          SZA
16          BUN HAVE_SZ
17          BUN GETSZ
18  HAVE_SZ, LDA IN_BUFFER
19          STA PROG_SIZE
20          CLA
21          STA IN_READY
22
23          LDA PROG_PHYS
24          STA PTR
25
26  L_LOOP, LDA PROG_SIZE
27          SZA
28          BUN L_READ
29          BUN L_RUN
30  L_READ, LDA IN_READY
31          SZA
32          BUN L_STORE

```

```

33      BUN L_READ
34  L_STORE, LDA IN_BUFFER
35          STA PTR I
36          ISZ PTR
37          CLA
38          STA IN_READY
39          LDA PROG_SIZE
40          ADD M_ONE
41          STA PROG_SIZE
42          BUN L_LOOP
43
44  L_RUN,  LDA PROG_PHYS
45          ATB
46          CLA
47          STA 0
48          RTI
49
50  SYSCALL, SZA
51          BUN SC_CHECK
52          BUN BOOT
53
54  SC_CHECK, ADD M_ONE
55          SZA
56          BUN SC_WRITE
57
58          ION
59  W_IN,  LDA IN_READY
60          SZA
61          BUN RD_DONE
62          BUN W_IN
63  RD_DONE,
64          LDA IN_BUFFER

```

```

65      STA MAILBOX
66      CLA
67      STA IN_READY
68      BUN SC_RET
69
70  SC_WRITE,
71          LDA MAILBOX
72          STA OUT_BUFFER
73          LDA ONE
74          STA OUT_READY
75          ION
76  W_OUT,  LDA OUT_READY
77          SZA
78          BUN W_OUT
79
80  SC_RET, IOF
81          LDA 030
82          STA 0
83          RTI
84
85  ISR,   STA SAVE_AC
86          CIL
87          STA SAVE_E
88          SKI
89          BUN I_OUT
90          INP
91          STA IN_BUFFER
92          LDA ONE
93          STA IN_READY
94  I_OUT, SKO
95          BUN I_END
96          LDA OUT_READY

```

```

97          SZA
98          BUN DO_OUT
99          BUN I_END
100 DO_OUT, LDA OUT_BUFFER
101          OUT
102          CLA
103          STA OUT_READY
104 I_END,  LDA SAVE_E
105          CIR
106          LDA SAVE_AC
107          RTI
108
109 ONE,   DEC 1
110 M_ONE, DEC -1
111 PROG_PHYS, HEX 300
112 PROG_SIZE, DEC 0
113 PTR,   HEX 0
114 IN_READY, DEC 0
115 IN_BUFFER, DEC 0
116 OUT_READY, DEC 0
117 OUT_BUFFER, DEC 0
118 SAVE_AC, DEC 0
119 SAVE_E, DEC 0
120
121          ORG 1000
122 MAILBOX, HEX 0
123          END


```

RTK vs Software Interrupt


```
1 ; user program
2
3 ORG      300
4
5 LDA      C_RD
6 RTK
7
8 LDA      MAILBOX
9 ADD      FIVE
10
11 STA      MAILBOX
12 LDA      C_WR
13 RTK
14
15 CLA
16 RTK      ;src/yic/yic90...
17
18 C_RD,    DEC 1
19 C_WR,    DEC 2
20 FIVE,    DEC 5
21
22          ORG 700
23
24 MAILBOX, DEC 0
```

```
1 mov ah, 0x0e
2
3 ; function number = 0Eh
4 ; : Display Character
5
6 mov al, '!'
7
8 ; AL = code of character
9 ; to display
10
11 int 0x10
12
13 ; call INT 10h,
14 ; BIOS video service
```

System Call

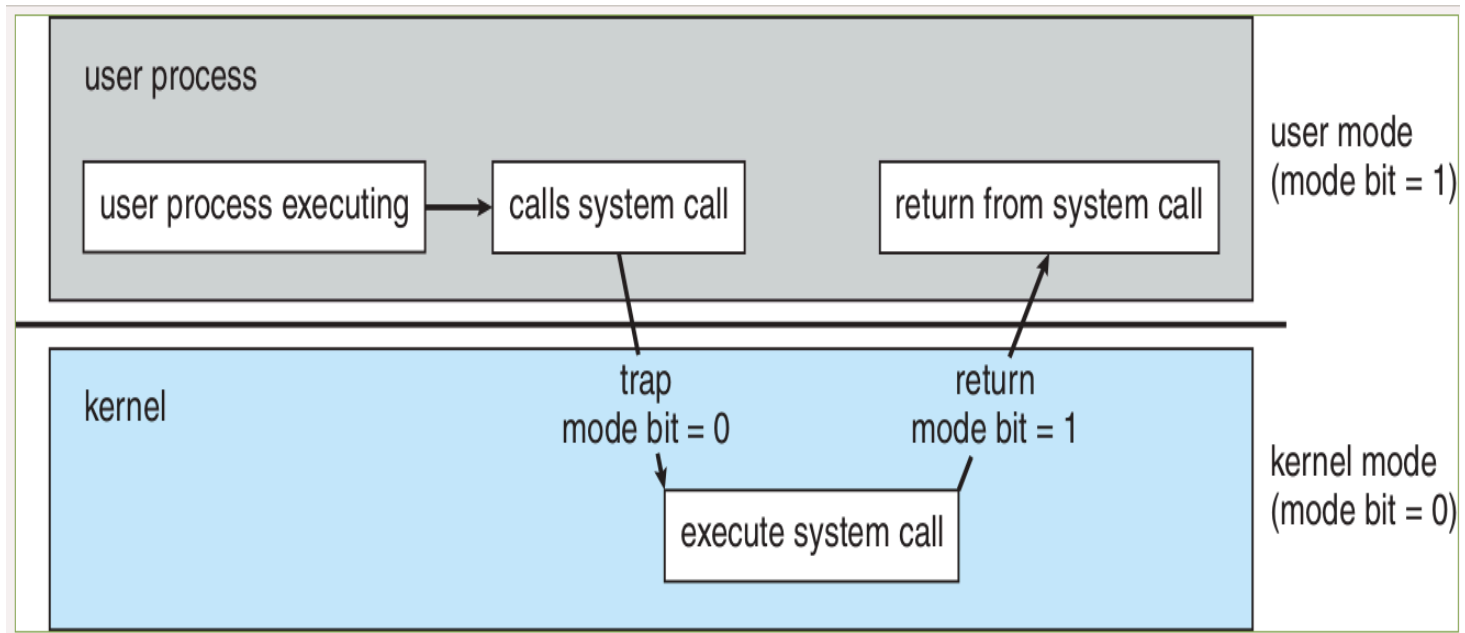


C System Call

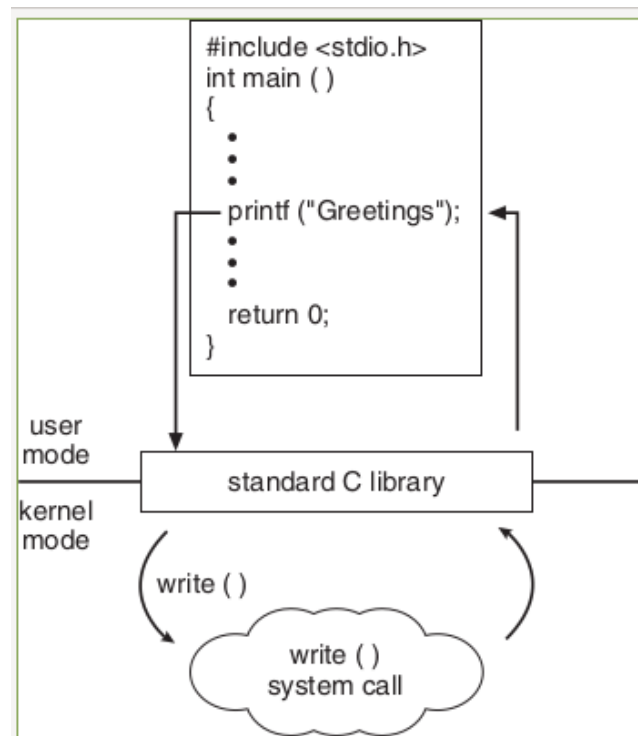

Timer interrupt

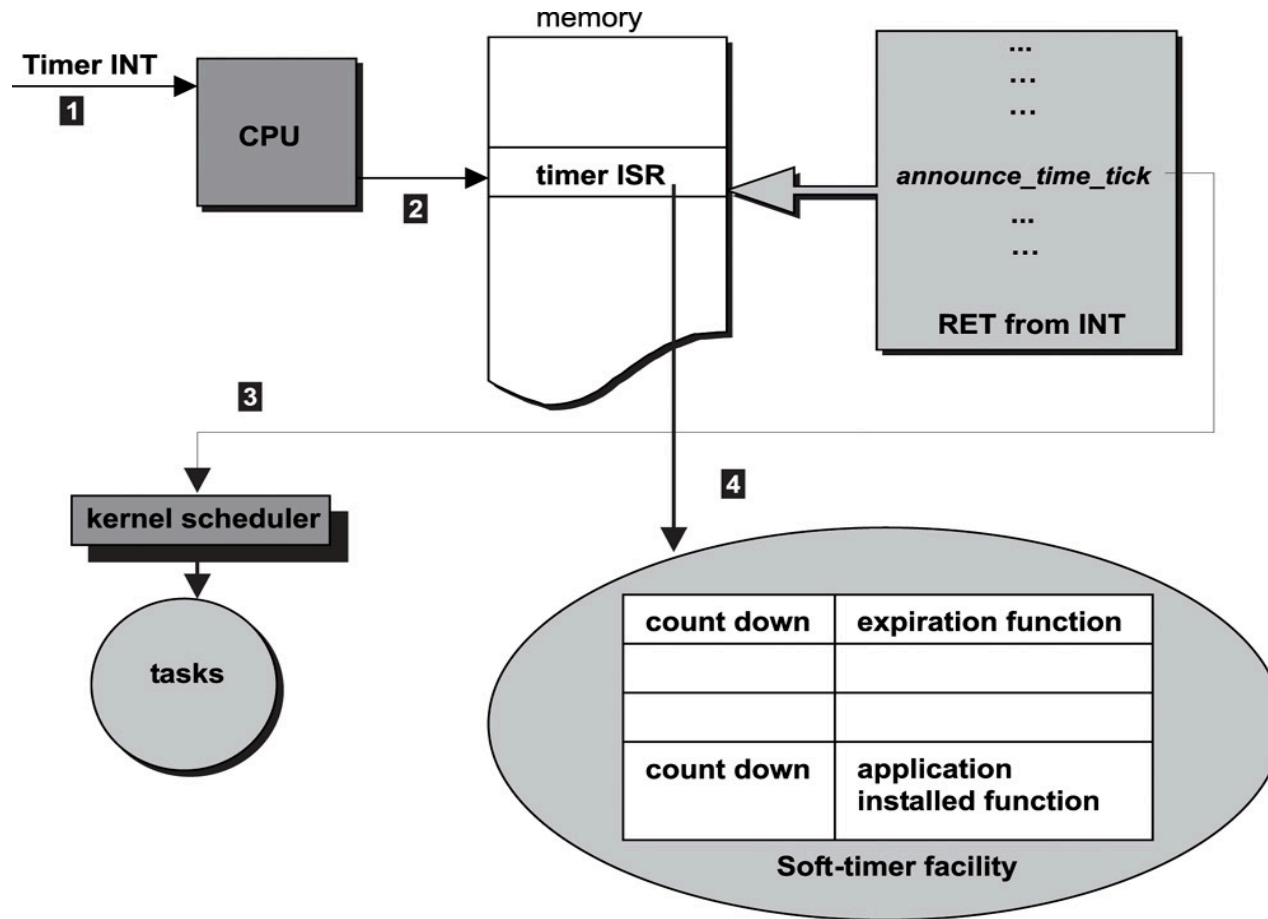The timer decrease by 1 at the start of every **Instruction Fetch Cycle**



Execution Time Limit Protection

- New Hardware Components
 - Timer Register (TR)
 - Timer Flag (FT)
- In user mode(MODE = 1)
 - TR-- for every instruction
 - If TR == 0, then FT $\leftarrow$ 1
- ATT (AC to Timer), TR $\leftarrow$ AC
- SKT (Skip on Timer Trap)
 - If FT == 1, then PC++, FT $\leftarrow$ 0
- Boot section

```
; ...  
; Read Card 1 into AC  
  
ATT  
  
; Read Card 2, program size  
; Read program cards  
; RTI to user program
```


- Interrupt Service Routine (ISR)

```
ISR,      STA      SAVE_AC  
          ; ... Save other things  
  
          SKT  
          BUN      CHECK_IO  
          BUN      TRAP_ABORT  
  
CHECK_IO, SKI  
          BUN      I_OUT  
  
          ; ...  
  
TRAP_ABORT,  
          ; took too long  
          ; end the program  
          BUN      BOOT
```

YIC 100

- User program can run ATT
- Privileged Instructions
- If $\text{MODE} == 1$
 - $\text{FT} \leftarrow 1$
 - $\text{SC} \leftarrow 0$
- else
 - $\text{TR} \leftarrow \text{AC}$
 - $\text{SC} \leftarrow 0$
- Other Privileged Instructions
- ATB
- RTI
- ION
- IOF
- INP
- OUT
- HLT
- Other Considerations
- trap for illegal instruction
 - Privileged
 - Non existence code
- CPU trap
 - timer expiration
 - illegal instruction

- Handling Leftover Cards

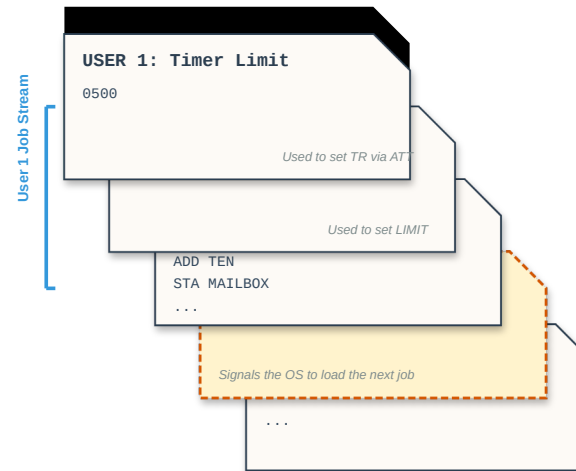

- Software solution (like old IBM JCL)
- Hardware Solution
 - CPU pulses a new output wire called **FLUSH**
 - Card Reader receives the FLUSH signal
 - Continuously feed and discard cards
 - Special sequence in a card
 - Raises the standard Input Flag $\text{FGI} \leftarrow 1$
 - FSH instruction to flush cards to next

YIC 100 Kernel code

```

1      BUN  BOOT
2      BUN  ISR
3      ORG  030
4      HEX  0
5      BUN  SYSCALL
6  BOOT,  CLA
7          STA  IN_READY
8          STA  OUT_READY
9          ION
10     L_TMR, LDA  IN_READY
11          SZA
12          BUN  HAVE_TMR
13          BUN  L_TMR
14  HAVE_TMR, LDA  IN_BUFFER
15          ATT
16          CLA
17          STA  IN_READY
18     L_SZ,  LDA  IN_READY
19          SZA
20          BUN  HAVE_SZ
21          BUN  L_SZ
22  HAVE_SZ, LDA  IN_BUFFER
23          STA  PROG_SIZE
24          CLA
25          STA  IN_READY
26          LDA  PROG_BASE
27          STA  PTR
28     L_LOOP, LDA  PROG_SIZE
29          SZA
30          BUN  L_READ
31          BUN  L_RUN
32     L_READ, LDA  IN_READY
33          SZA

```

```

35      BUN  L_STORE
36      BUN  L_READ
37     L_STORE, LDA  IN_BUFFER
38          STA  PTR I
39          ISZ  PTR
40          CLA
41          STA  IN_READY
42          LDA  PROG_SIZE
43          ADD  M_ONE
44          STA  PROG_SIZE
45          BUN  L_LOOP
46     L_RUN,  LDA  PROG_BASE
47          ATB
48          CLA
49          STA  0
50          RTI
51     SYSCALL, SZA
52          BUN  SC_CHECK
53     SC_EXIT, FSH
54          BUN  BOOT
55     SC_CHECK, ADD  M_ONE
56          SZA
57          BUN  SC_WRITE
58          ION
59     W_IN,  LDA  IN_READY
60          SZA
61          BUN  RD_DONE
62          BUN  W_IN
63     RD_DONE, LDA  MAIL_PHYS
64          STA  PTR
65          LDA  IN_BUFFER
66          STA  PTR I

```

```

67      CLA
68      STA  IN_READY
69      BUN  SC_RET
70     SC_WRITE,
71          LDA  MAIL_PHYS
72          STA  PTR
73          LDA  PTR I
74          STA  OUT_BUFFER
75          LDA  ONE
76          STA  OUT_READY
77          ION
78     W_OUT, LDA  OUT_READY
79          SZA
80          BUN  W_OUT
81     SC_RET, IOF
82          LDA  030
83          STA  0
84          RTI
85     ISR,  STA  SAVE_AC
86          CIL
87          STA  SAVE_E
88          SKT
89          BUN  CHK_IO
90          BUN  BOOT
91     CHK_IO, SKI
92          BUN  CHK_OUT
93          INP
94          STA  IN_BUFFER
95          LDA  ONE
96          STA  IN_READY
97     CHK_OUT, SKO
98          BUN  ISR_END

```

```

99      LDA  OUT_READY
100      SZA
101      BUN  DO_OUT
102      BUN  ISR_END
103 DO_OUT, LDA  OUT_BUFFER
104          OUT
105          CLA
106          STA  OUT_READY
107     ISR_END, LDA  SAVE_E
108          CIR
109          LDA  SAVE_AC
110          ION
111          RTI
112 ONE,          DEC  1
113 M_ONE,        DEC  -1
114 PROG_BASE,   HEX  300
115 MAIL_PHYS,   HEX  1000



```

```


1      LDA  C_RD
2      RTK
3      LDA  MAILBOX
4      ADD  TEN
5      STA  MAILBOX
6      LDA  C_WR
7      RTK
8      CLA
9      RTK
10     C_RD,    DEC  1
11     C_WR,    DEC  2
12     TEN,     DEC  10
13          ORG  700
14     MAILBOX, DEC  0

```

Ordinary CPUs

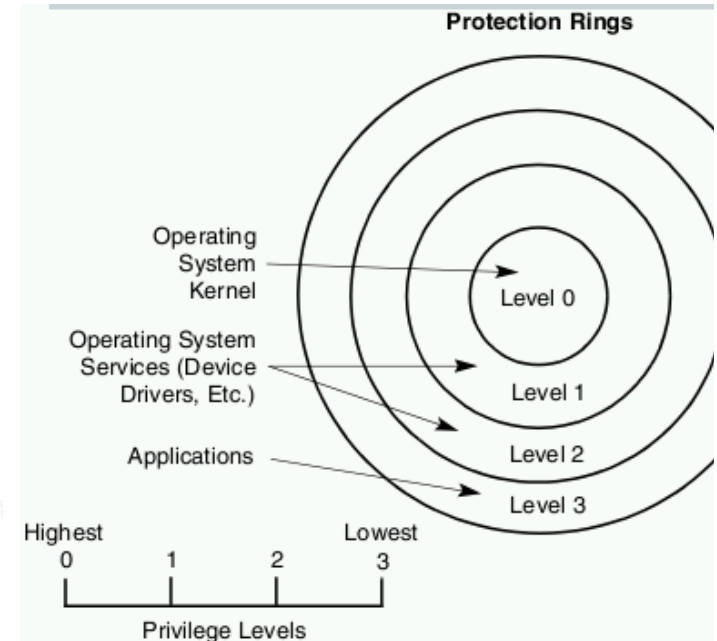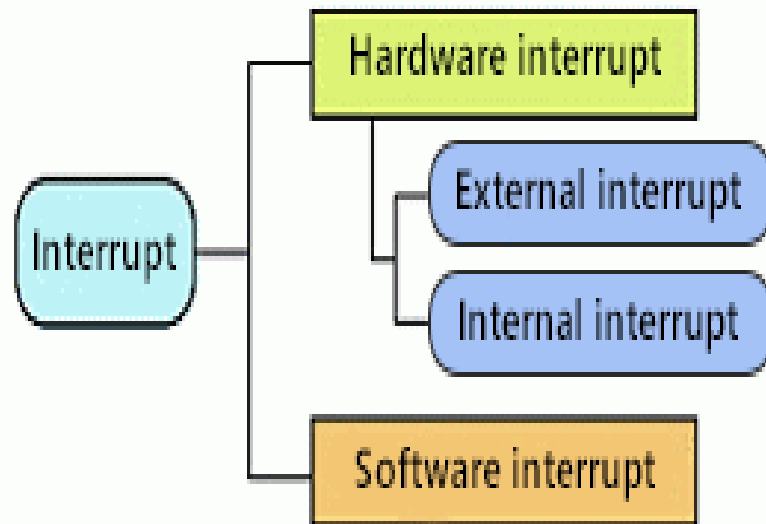

YIC 110 Memory Protection

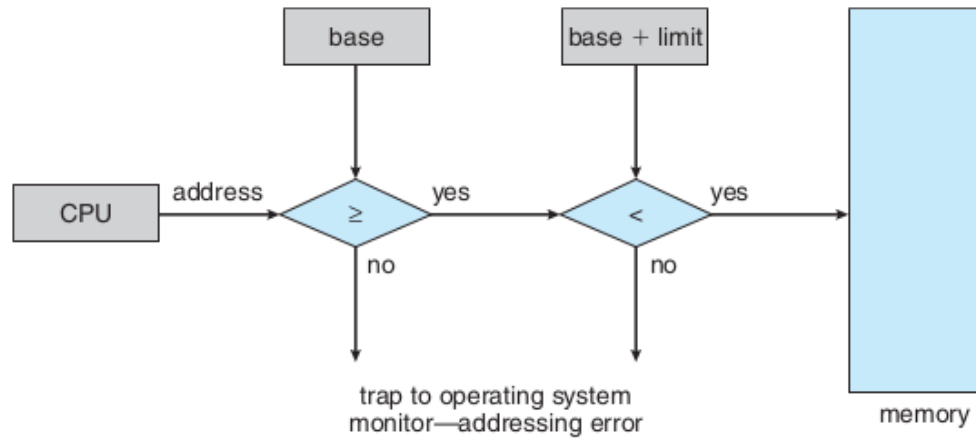

BSA problem for multiprogramming


- General cons of BSA
 - No recursion
 - No explicit data transfer

Function call

- Stack register
- CALL
- RET
- PUSH
- POP

Stack From end

Call, Ret

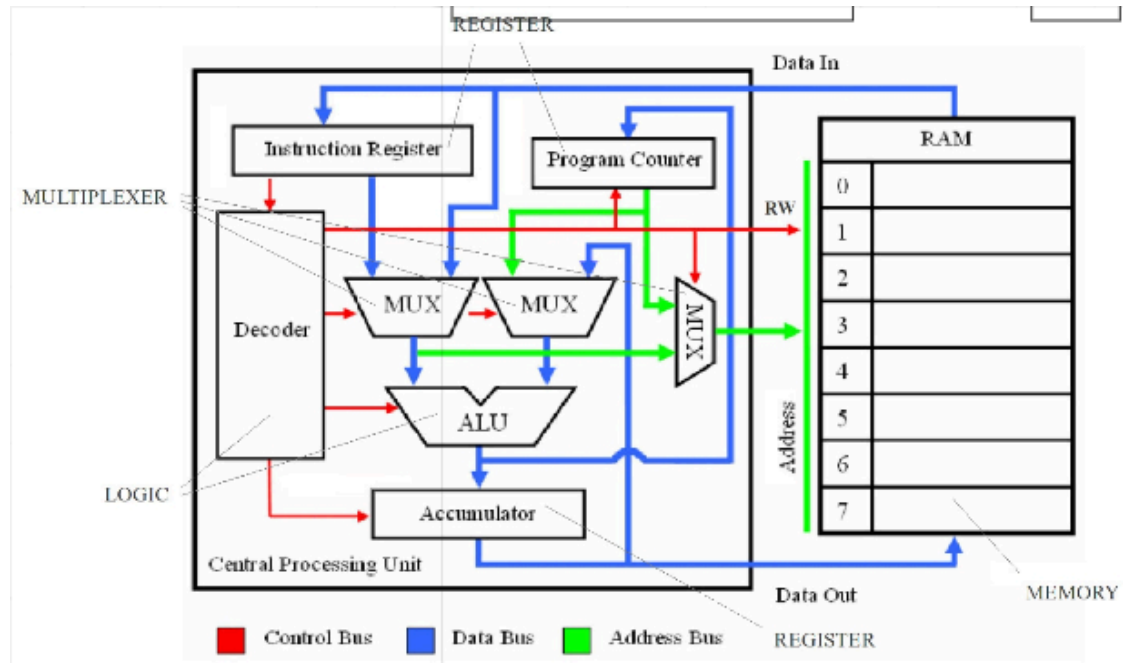

- Assembly Slides


Adding PSW

Flags:


- Carry
- E
- Mode

YIC 150 - Multiprogramming


Process along Printer Function

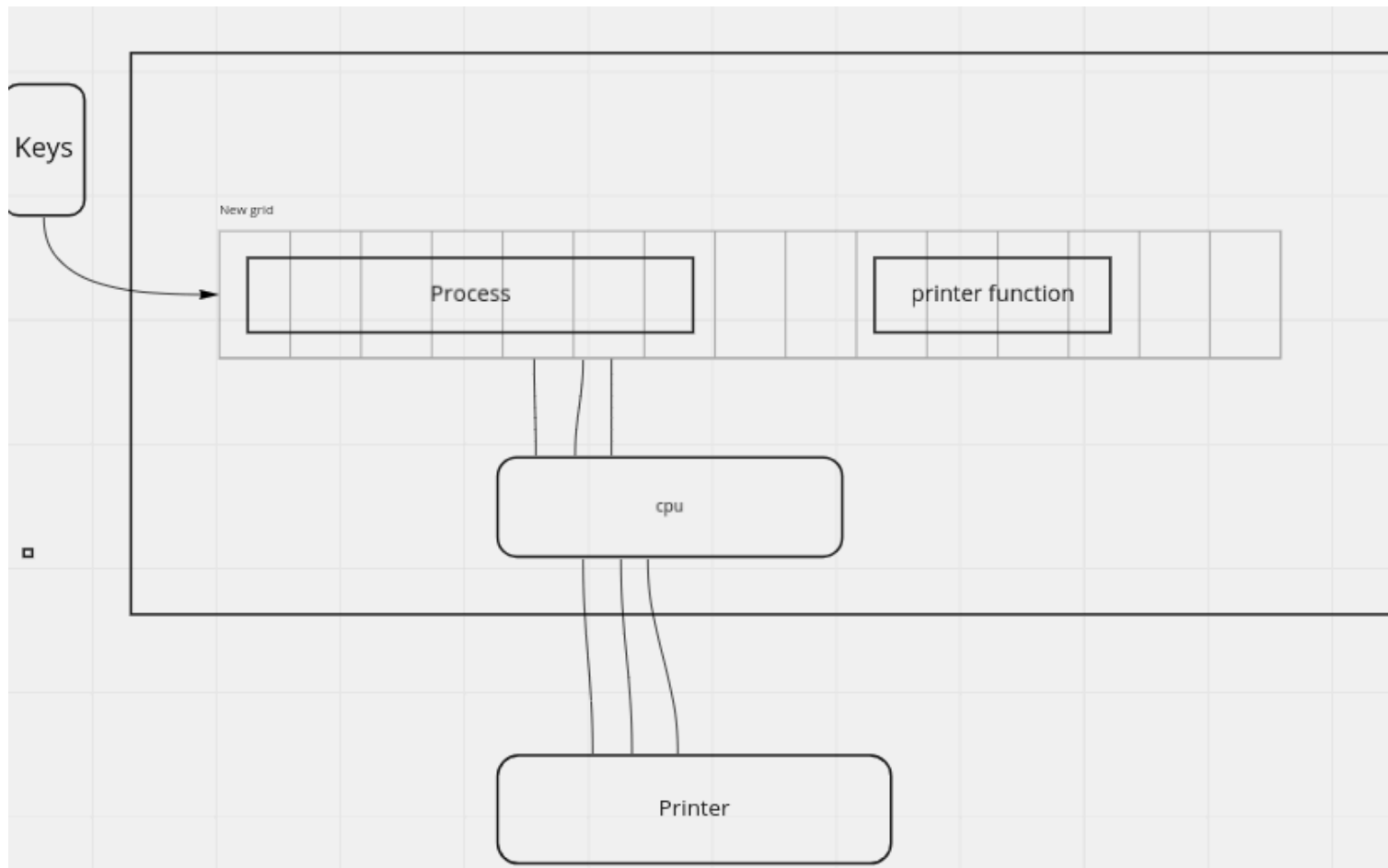


Jump to Printer Procedure

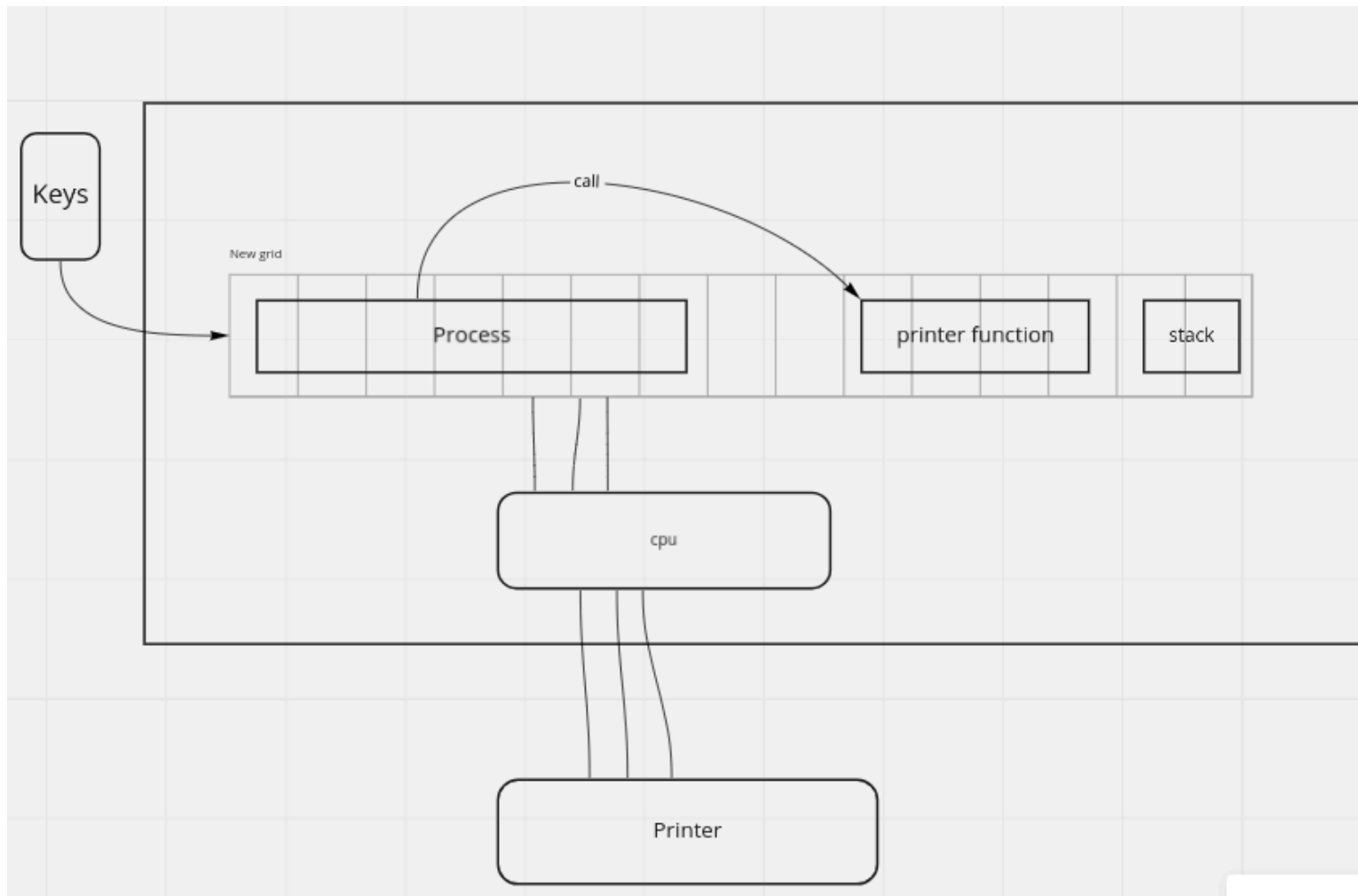


Return from Printer Procedure

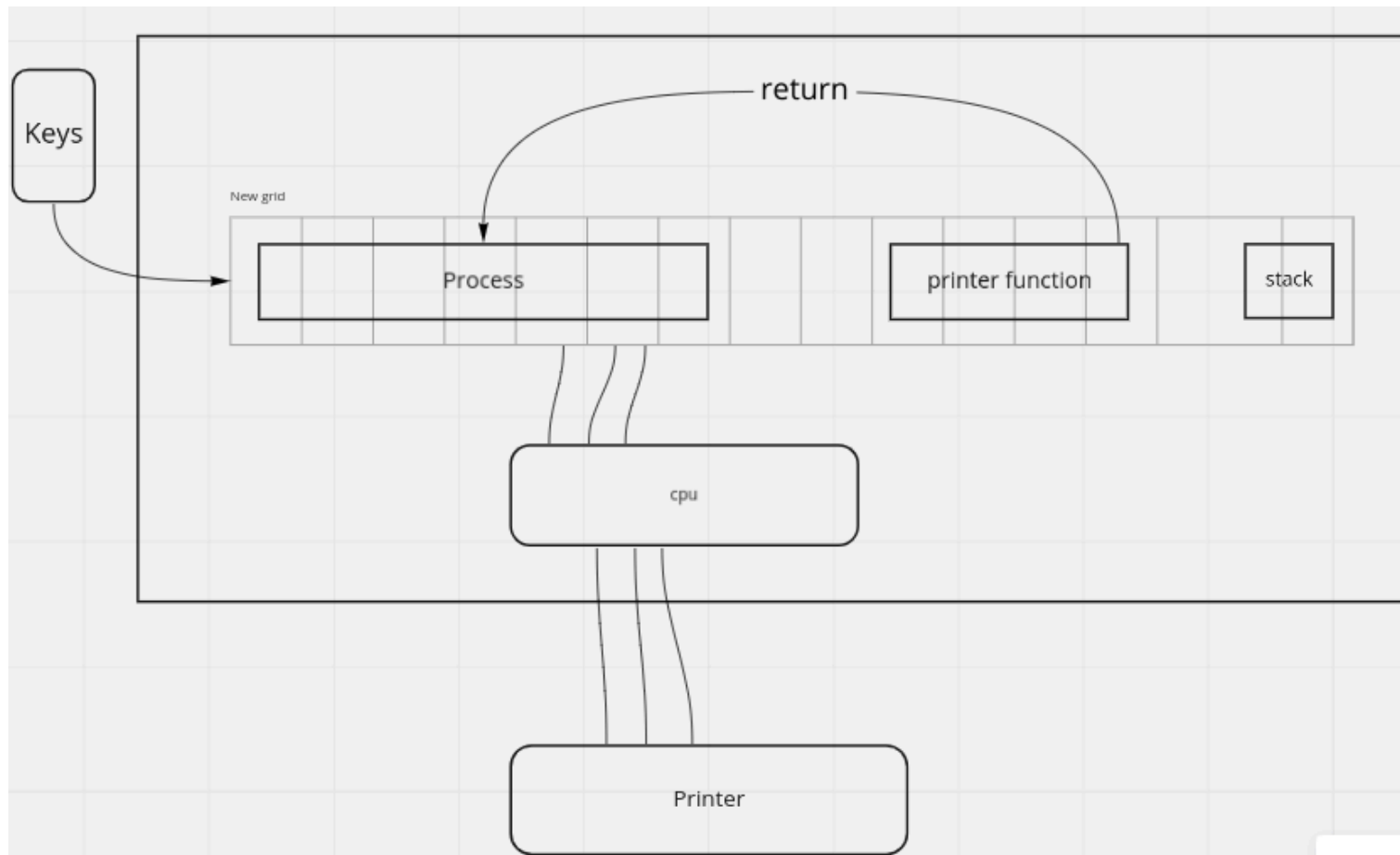

Display and Printer Procedure

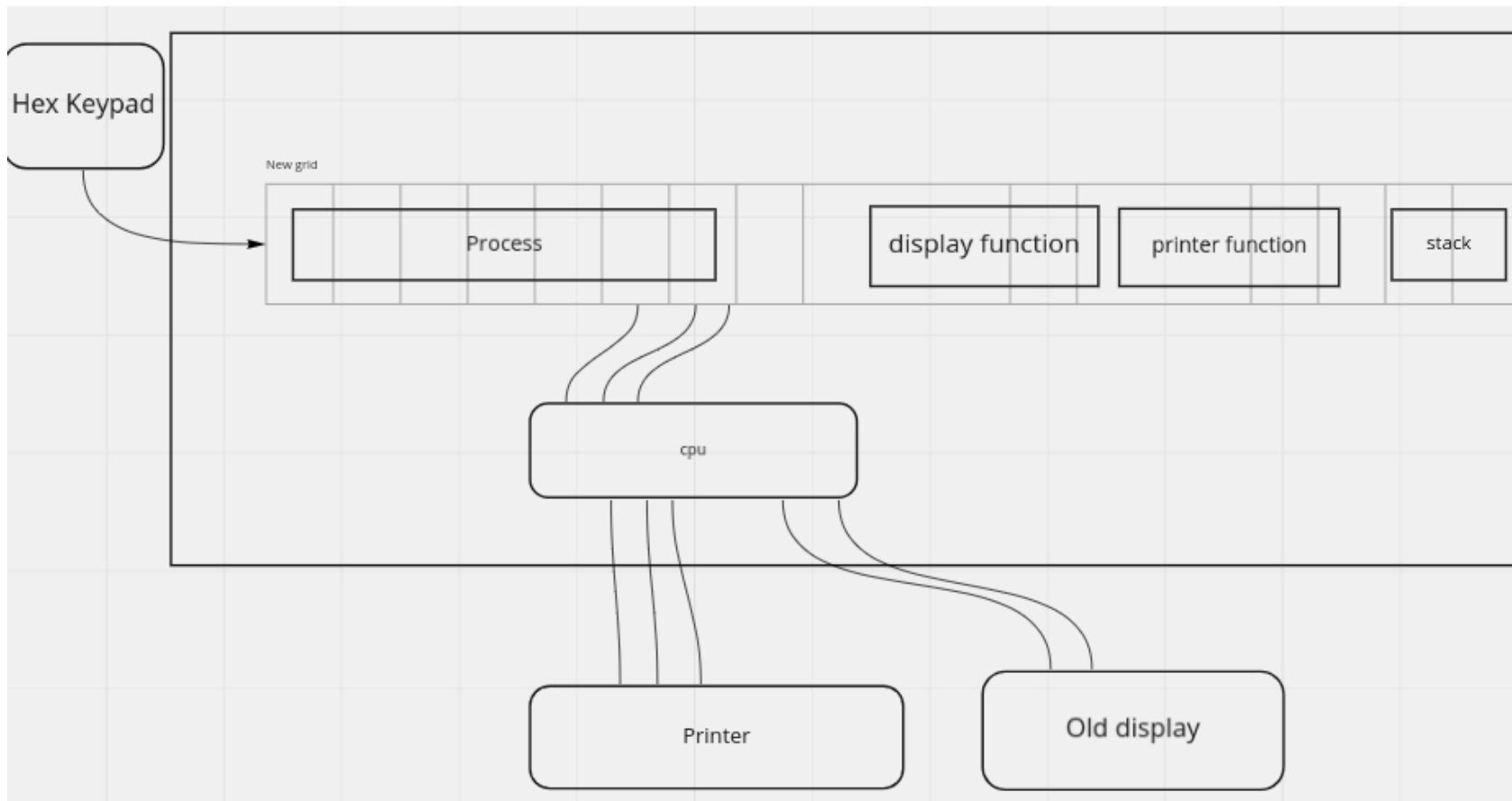


BIOS

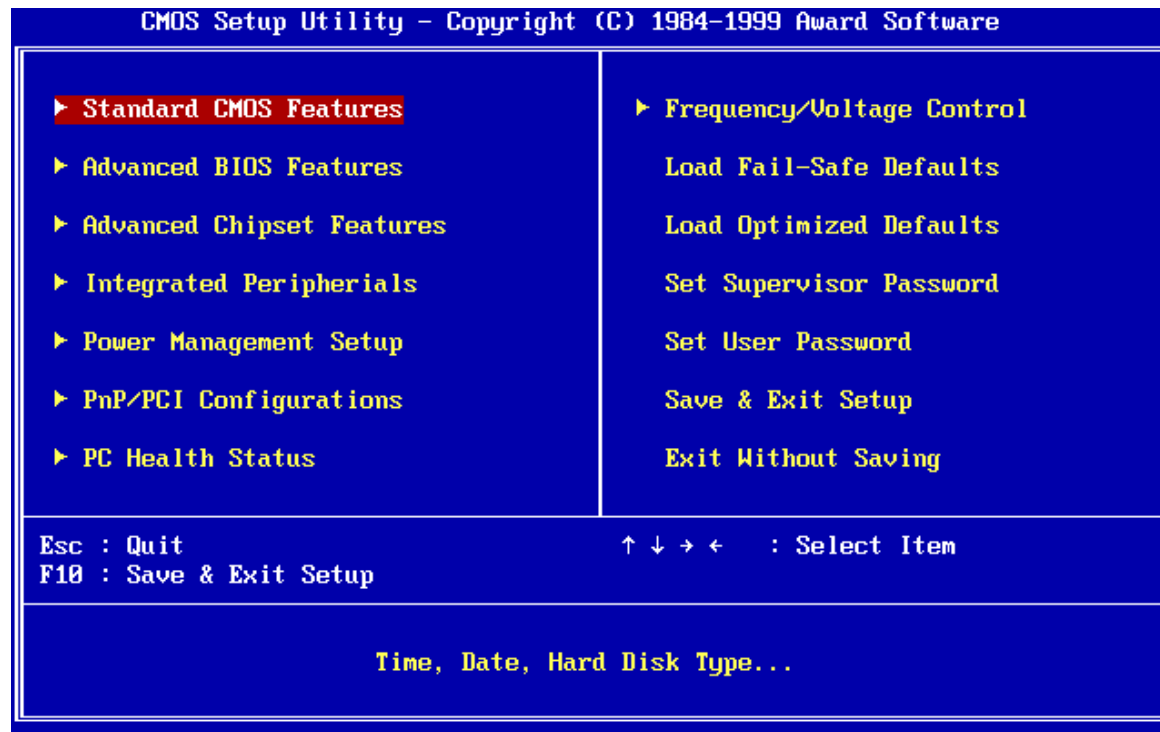

Main Security System Configuration Exit	
System Time	[22:58:20]
System Date	[07/26/2016]
Product Name	HP ENVY x360 Convertible 13-y0XX
Product Number	YODSKU1#ABA
System Board ID	82B7
Born On Date	07/25/2016
Processor Type	Intel(R) Core(TM) i7-750U CPU @ 2.70GHz
Total Memory	16 GB
BIOS Version	B.09
BIOS Vendor	American Megatrends
Serial Number	36444335-3432-5842-3053-535834324435
UUID Number	PYD4F018J30019
System Board CT Number	Win10
Factory installed OS	24852 05/26/2016
Primary Battery SN	
► System Log	
Build ID	16WW3DST6A#SABA#DABA
Feature Byte	3K6b 7K7N 7WaB apaq asau awbV bhhbz cbdU dXdp dqew .E5
F1 Help ↑↓ Select Item F5/F6 Change Values	


Boot sequence

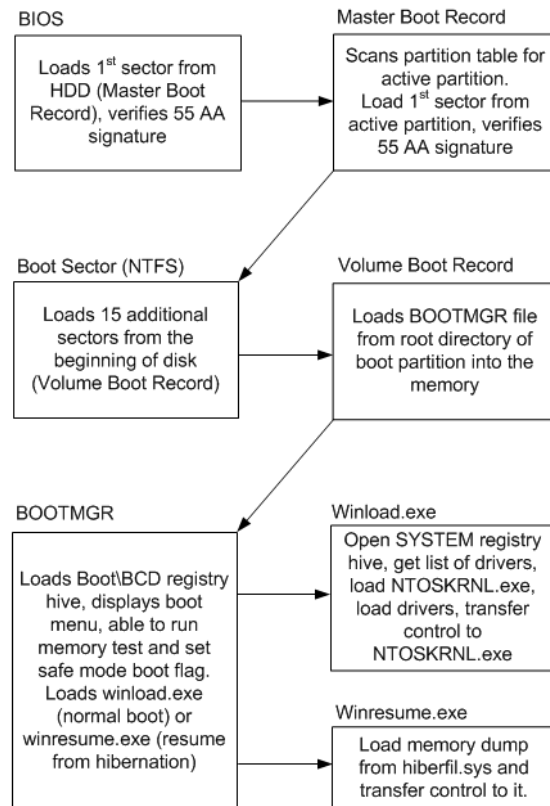

```
Ubuntu 8.04, kernel 2.6.24-16-generic
Ubuntu 8.04, kernel 2.6.24-16-generic (recovery mode)
Ubuntu 8.04, memtest86+
Other operating systems:
Windows Vista/Longhorn (loader)
```

Use the ↑ and ↓ keys to select which entry is highlighted.
Press enter to boot the selected OS, 'e' to edit the
commands before booting, or 'c' for a command-line.

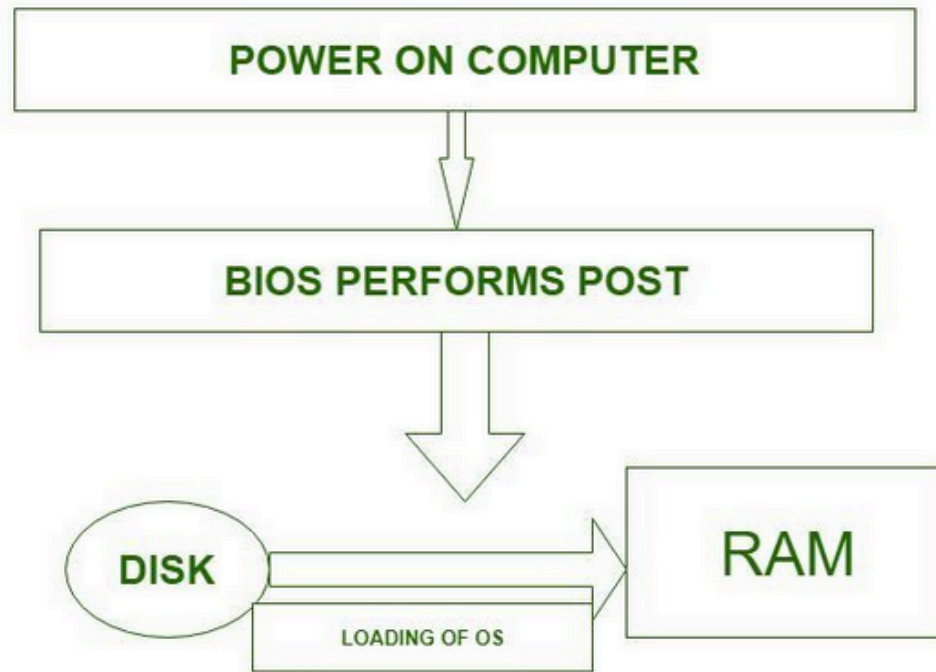
The highlighted entry will be booted automatically in 4 seconds.




- [IEEE Std 1275 1994 Standard for boot initialization](#)
- [https://openfirmware.info/Welcome to OpenBIOS](https://openfirmware.info/Welcome_to_OpenBIOS)
- <https://github.com/openbios>
- <https://github.com/openbios/openbios>

YIC120 - Adding Keyboard & Disk

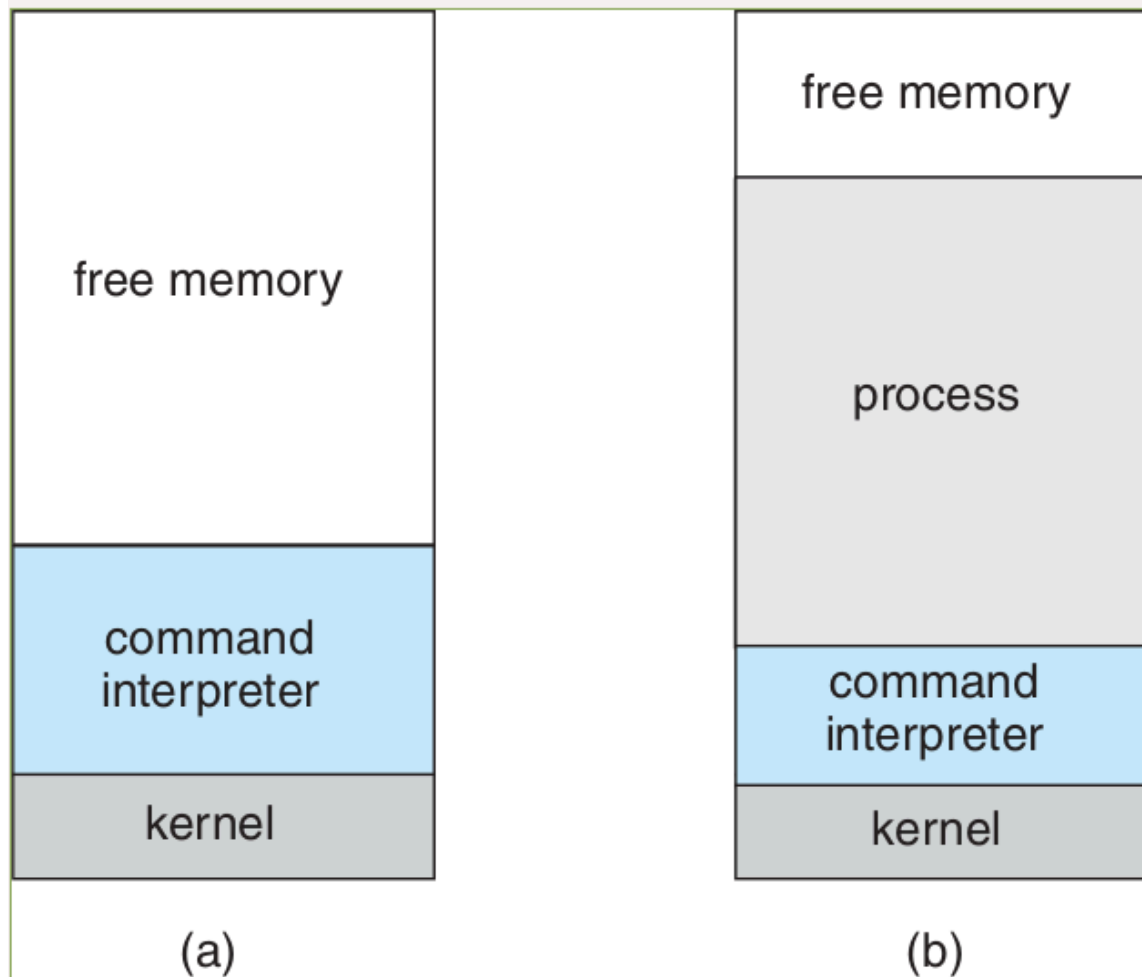- terminal (command prompt)
- batch system
- interactive system



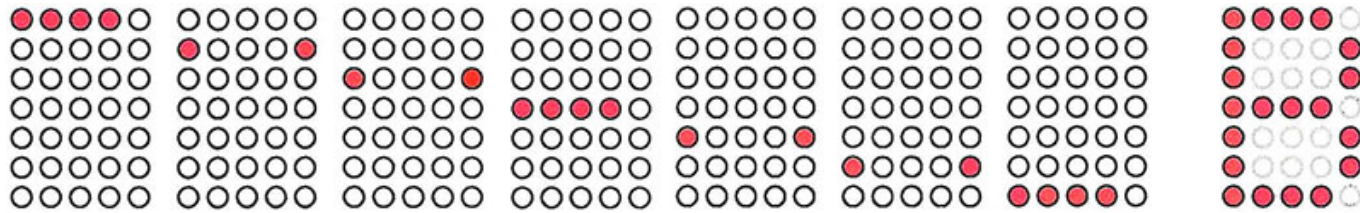When a controller rapidly turns on LEDs in one row at a time



<https://www.nutsvolts.com/magazine/article/create-an-led-sign-controller>

Context Switch

END

